

Problem 1: Apply DC techniques to solve the following circuits

- a) Use nodal voltage analysis to find v_o in the circuit shown in Figure 1. (10 Marks)

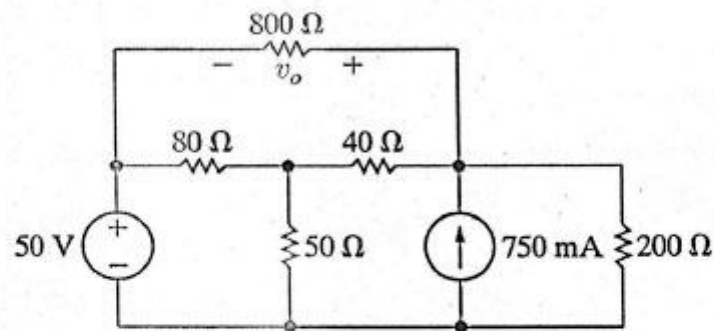


Figure 1

- b) Use mesh current analysis to find v_o in the circuit shown in Figure 2. (10 Marks)

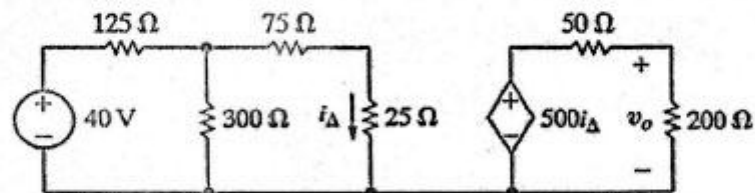


Figure 2

- c) Use the principle of superposition to find i_o in Figure 3. (5 Marks)

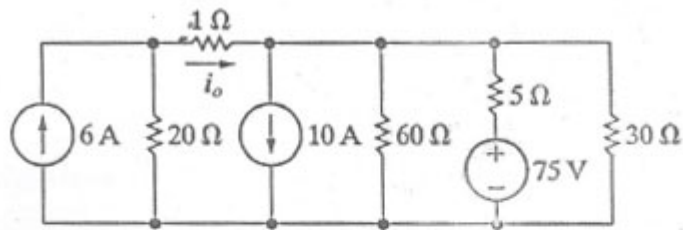


Figure 3

Problem 2: Apply DC techniques to solve the following circuits

- a) Make a series of source transformations to find the voltage v_o in Figure 4. (5 Marks)

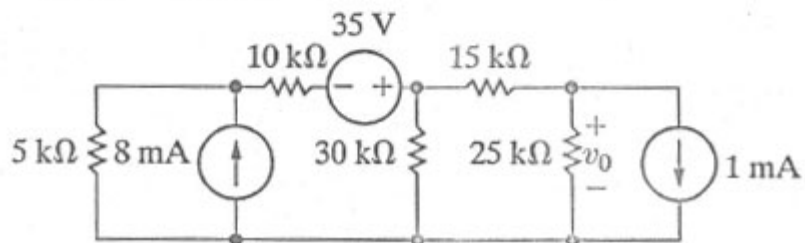


Figure 4

- b) Find R_{eq} and i_o in the circuit in Figure 5. (5 Marks)

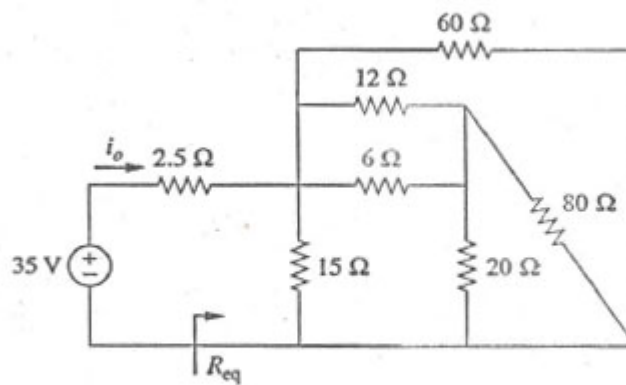


Figure 5

- c) In the circuit shown in Figure 6, find

- Thevenin's equivalent circuit between terminals a and b.
- The value of R_o that achieves maximum power transfer.
- The value of maximum power that can be delivered to R_o .

(10 Marks)

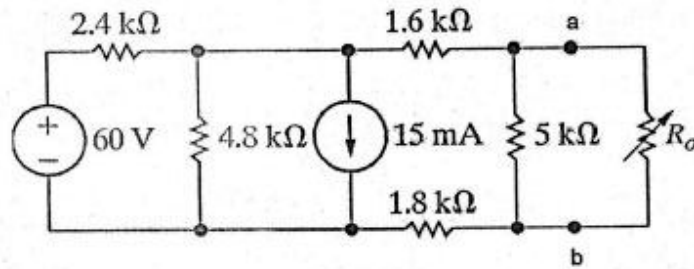


Figure 6

- d) Find i_L in the circuit shown in Figure 7 (5 Marks)

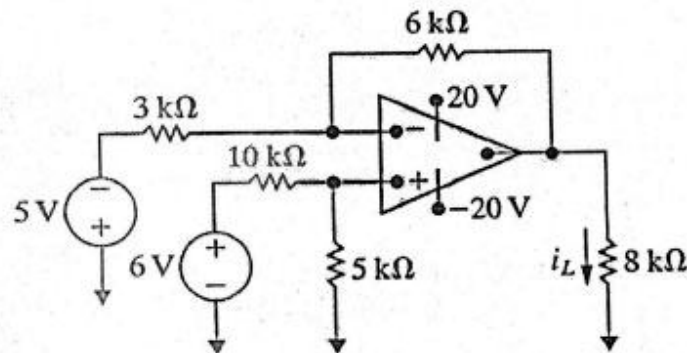


Figure 7

Problem 3: Solve the following first order or second order circuits

- a) The switch in the circuit in Figure 8 has been in position 1 for a long time. At $t=0$ the switch moves instantaneously to position 2. Find $v_o(t)$ for $t > 0$. (7.5 Marks)

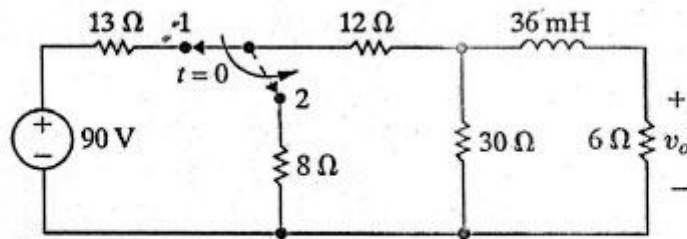


Figure 8

- b) The switch in Figure 9 was closed at $t=0$ after being open for a long time. Find:
- $i_1(t)$ for $t > 0$
 - $i_2(t)$ for $t > 0$

(7.5 Marks)

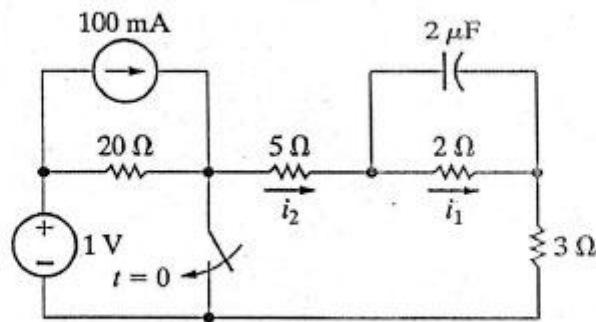


Figure 9

- c) In the circuit shown in Figure 10, the resistor is chosen such that the circuit is critically damped. The initial capacitor voltage is 15 V and the initial inductor current is 6 mA. Find the value of R , then find $v_c(t)$ and $i(t)$ for $t > 0$. (10 Marks)

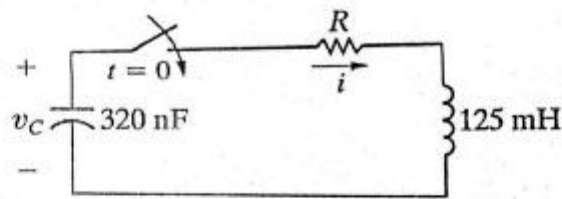


Figure 10

Problem 4: Solve the following AC problems

- a) Find the input admittance for the circuit shown in Figure 11. (5 Marks)

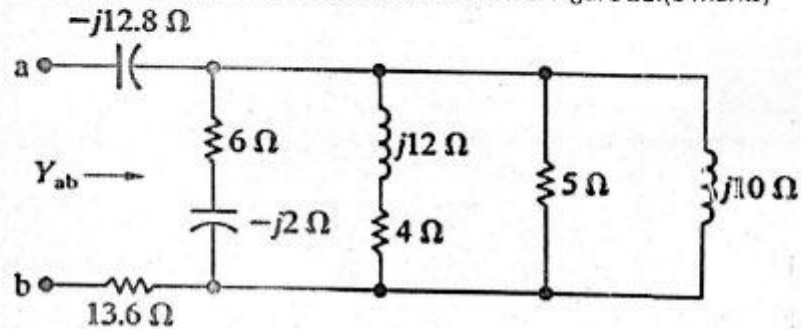


Figure 11

- b) Use source transformations to find thevenin's equivalent circuit between terminal a and b in Figure 12. (5 Marks)

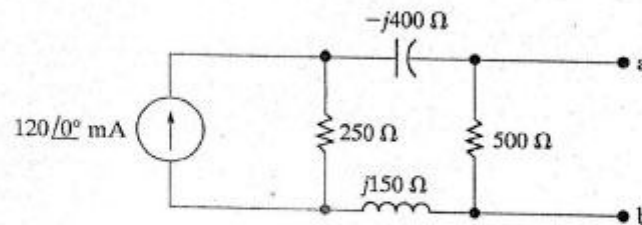


Figure 12

- c) Use nodal analysis to find the voltage V_g and current I_g in the circuit shown in Figure 13. Then find the complex power supplied by the voltage source and current source. (10 Marks)

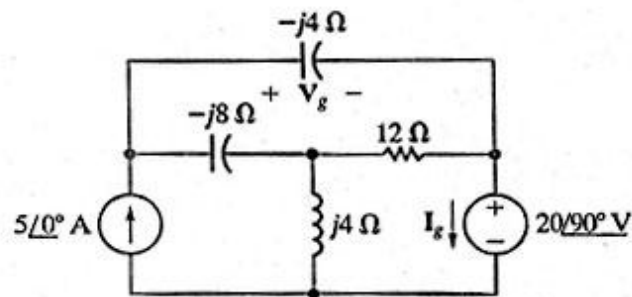


Figure 13

- d) Three loads are connected in parallel to a $120 \angle 0^\circ \text{ V}$ source. Load 1 absorbs 60 kVAR at $\text{pf}=0.85$ lagging, load 2 absorbs 90 kW and 50 kVAR leading, and load 3 absorbs 100 kW at $\text{pf}=1$.
- Find the equivalent impedance.
 - Calculate the power factor of the parallel combination.
 - Determine the current supplied by the source.

(5 Marks)