

Problem (3) [10 points]

For the feedback amplifier given in Fig. 3. $A_g=100\text{mA/V}$, $R_i=10\text{K}\Omega$, $R_o=10\text{K}\Omega$, $\beta_z=0.1\text{k}\Omega$.

- Identify the type of the feedback
- Derive the expression for the closed loop gain $A_{gf}=I_o/V_s$, and determine its value.
- Derive the expression for the closed loop input resistance R_{if} , and determine its value.
- Derive the expression for the closed loop output resistance R_{of} , and determine its value.
- Comment on the effect of the feedback on the input and output resistances (increased or decreased)

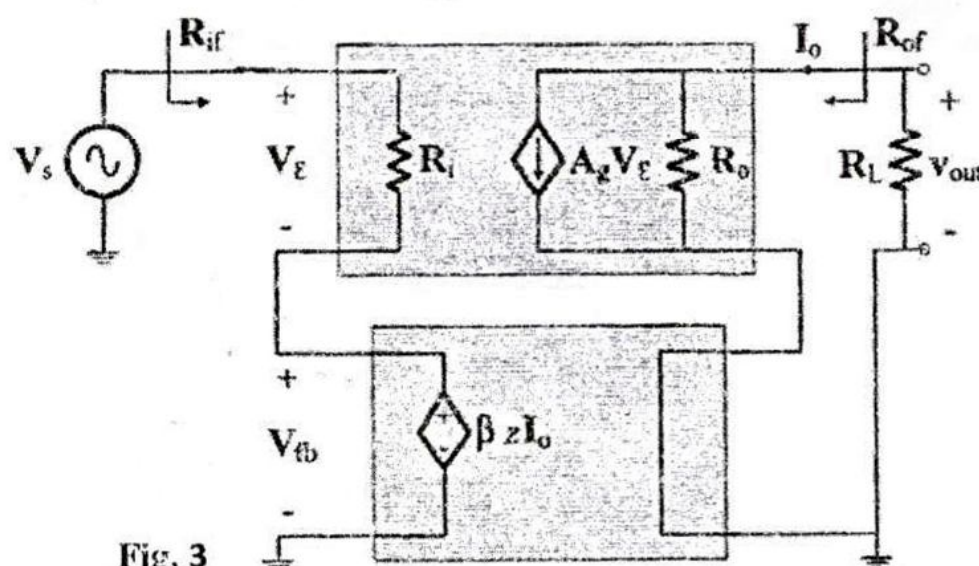


Fig. 3

Problem (4) [15 points]

For the following circuit in Fig. 4, the transistor parameters are: $I_{CQ1}=486\mu\text{A}$ and $I_{CQ2}=1.35\text{mA}$, $g_{m1}=19.64\text{mA/V}$, $g_{m2}=34.92\text{mA/V}$, $r_{\pi1}=5092\Omega$, $r_{\pi2}=2857\Omega$, $r_{o2}=r_{o1}=\infty$.

- Identify the topology of the feedback (mixing/sampling).
- Identify the feedback circuit, then find values for R_{11} , R_{22} , and the feedback parameter β_{FB} .
- Drew the amplifier without the FB including the effect of R_{11} and R_{22} . Then, find the amplifier Transresistance gain $R_m = \frac{v_o}{i_s}$.
[Hint: use source transformation to get i_s from v_s]
- Find the closed-loop gain R_{mf} , then use current voltage relations to find the voltage gain $A_{vf} = \frac{v_o}{v_s}$.
- Find the input resistance R_{in} and the output resistance R_o (as indicated in the opposite figure).

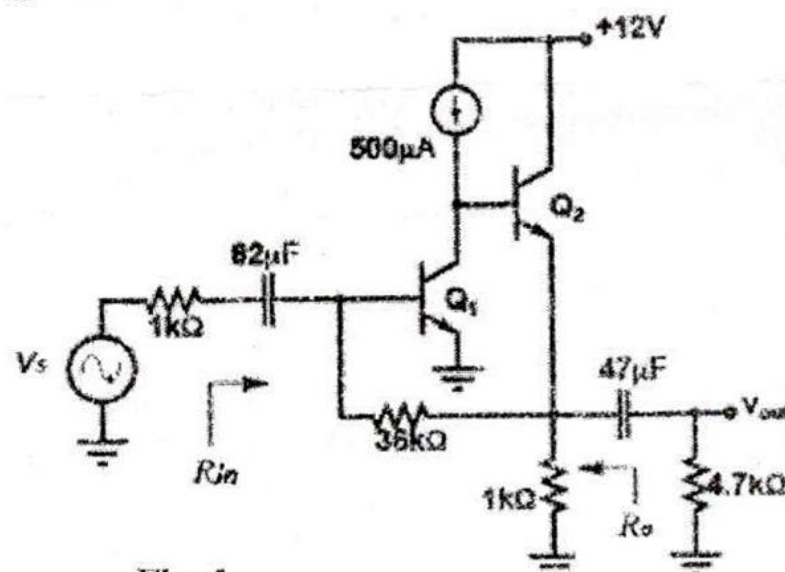


Fig. 4

Problem (5) [15 points]:

For the emitter follower output stage shown below, $V_{cc}=-V_{EE}=2.5\text{V}$, $V_{CE,sat}=0.2\text{V}$, $V_{BE,on}=0.7\text{V}$, $R_L=10\text{k}\Omega$.

- Classify this power amplifier.
- Find the value of R_1 that results in maximum efficiency.
- Draw the transfer function (v_{OUT} versus v_{IN}).
- Determine the resulting output voltage swing and the maximum and minimum Q_1 emitter currents, i_{E1} .
- Calculate the Average power delivered by the batteries, and the power delivered to the load.
- Calculate maximum power conversion efficiency.

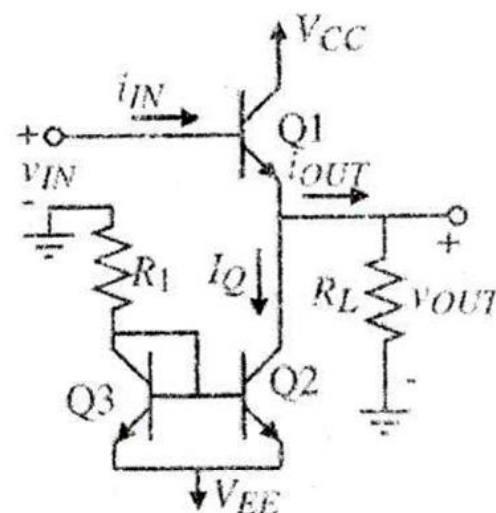


Fig. 5